

# PHYSICS 1B QUIZ #3 FALL QUARTER 2009

Form A

YOUR NAME \_\_\_\_\_ Answer Key \_\_\_\_\_ (PRINT NEATLY!)

YOUR PID NUMBER \_\_\_\_\_ (PRINT NEATLY!)

**INSTRUCTIONS: THERE ARE 10 QUESTIONS ON THIS QUIZ. PLEASE FILL IN THE SCANTRON FORM USING A NUMBER 2 PENCIL.** *Note: Any confirmed case of cheating will result in an "F" grade in Physics 1B and referral to the dean for disciplinary action.*

1. A 20- $\Omega$  platinum wire at 20°C with a temperature coefficient of resistivity of  $3.9 \times 10^{-3} (\text{°C})^{-1}$  will have what resistance at 100°C?

$$R = R_0[1 + \alpha(T - T_0)]$$
$$R = 20[1 + 3.9 \times 10^{-3}(80)] = 26\Omega$$

- a. 14  $\Omega$   
b. 20  $\Omega$   
c. 26  $\Omega$   
d. 28  $\Omega$
2. A turbine at an electric power plant delivers 4,500 kW of power to an electrical generator which converts 95% of this mechanical energy into electrical energy. What is the current delivered by the generator if it delivers at 3,600 V?

$$W = \frac{95}{100} \times 4500 \times 10^3 = 4.28E6$$
$$W = I \times \Delta V \Rightarrow I = \frac{4.28E6}{3600} = 1.2E3$$

- a.  $0.66 \times 10^3$  A  
b.  $1.0 \times 10^3$  A  
c.  $1.2 \times 10^3$  A  
d.  $5.9 \times 10^3$  A
3. Number 10 copper wire (radius = 1.3 mm) is commonly used for electrical installations in homes. What is the voltage drop in 40 m of #10 copper wire if it carries a current of 10 A? (The resistivity of copper is  $1.7 \times 10^{-8} \Omega \cdot \text{m}$ .)

$$R = \rho \frac{l}{A} = 1.7 \times 10^{-8} \frac{40}{\pi(1.3E-3)^2} = 0.13\Omega$$
$$V = IR = 10 \times 0.13 = 1.3 V$$

- a. 1.3 V  
b. 0.77 V  
c. 0.50 V  
d. 0.13 V

4. A high voltage transmission line of diameter 2 cm and length 200 km carries a steady current of 1 000 A. If the conductor is copper with a free charge density of  $8 \times 10^{28}$  electrons/m<sup>3</sup>, how long does it take one electron to travel the full length of the cable? ( $e = 1.6 \times 10^{-19}$  C)

$$I = nqv_d A \Rightarrow v_d = \frac{1000}{8 \times 10^{28} \times 1.6E - 19 \times \pi \times 10^4} = 2.49E - 4 \frac{m}{s}$$

$$x = Vt \Rightarrow t = \frac{200 \times 10^3}{2.49E - 4} = 8 \times 10^8$$

- a.  $8 \times 10^2$  s
- b.  $8 \times 10^4$  s
- c.  $8 \times 10^6$  s
- d.  $8 \times 10^8$  s

5. A resistor is made of a material that has a resistivity that is proportional to the current going through it. If the voltage across the resistor is doubled, what happens to the power dissipated by it?

$$\rho \propto I, V' \rightarrow 2V, V = IR \Rightarrow I' \rightarrow \sqrt{2} \text{ \& } R' \rightarrow \sqrt{2}$$

$$W = IV \Rightarrow W' = I'V' \Rightarrow 2 \times \sqrt{2}IV = 2^{3/2}$$

- a. It doubles.
- b. It quadruples.
- c. It increases by a factor of  $2^{3/2}$ .
- d. It increases by a factor of  $2^{1/2}$ .

6. Three resistors connected in parallel have individual values of 4.0, 6.0 and 10.0  $\Omega$ , respectively. If this combination is connected in series with a 12-V battery and a 2.0-  $\Omega$  resistor, what is the current in the 10-  $\Omega$  resistor?

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{4} + \frac{1}{10} \Rightarrow R = 1.94\Omega$$


$$R_{tot} = 1.94 + 2 = 3.94\Omega$$

$$I_{tot} = \frac{12}{3.94} = 3.05 \text{ A}$$

$$V \text{ of } 10\Omega \text{ resistor} = 1.94 \times 3.05 = 5.92V$$

$$\text{The current in the } 10\Omega \text{ is } I = \frac{5.92}{10} = 0.59A$$

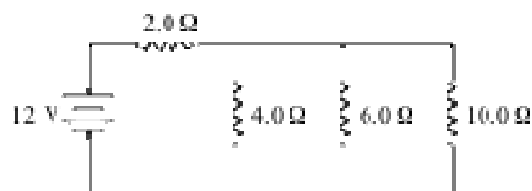
- a. 0.59 A
- b. 1.0 A
- c. 11 A
- d. 16 A



7. A 1 000-V battery, a 3 000-  $\Omega$  resistor and a 0.50- $\mu$ F capacitor are connected in series with a switch. The time constant for such a circuit, designated by the Greek letter,  $\tau$ , is defined as the time required to charge the capacitor to 63% of its capacity after the switch is closed. What is the value of  $\tau$  for this circuit?

$$\tau = RC = 3000 \times 0.5E - 6 = 1.5E - 3 s$$

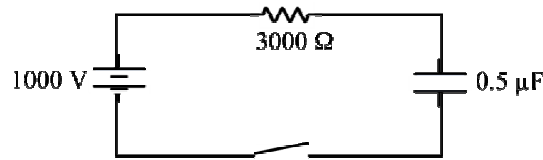- a.  $6.0 \times 10^9 s$
- b.  $1.7 \times 10^{-10} s$
- c.  $1.7 \times 10^{-7} s$
- d.  $1.5 \times 10^{-3} S$




8. If  $\mathcal{E} = 20 V$ , at what rate is thermal energy being generated in the 20-  $\Omega$  resistor?

$$\frac{1}{R} = 3 \times \frac{1}{30} \Rightarrow R = 10\Omega$$

$$R_{tot} = 10 + 20 + 40 = 70\Omega$$

$$I_{tot} = \frac{20}{70} = 0.3A \Rightarrow W = IR^2 = 0.29 \times 20^2 = 1.6W$$

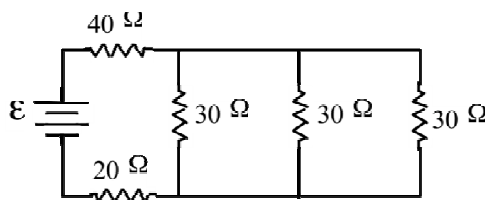- a. 6.5 W
- b. 1.6 W
- c. 15 W
- d. 26 W



9. If  $I = 2.0 \text{ mA}$  and the potential difference,  $V_A - V_B = +30 \text{ V}$  in the circuit segment shown, determine the charge and polarity of the capacitor.

$$\frac{q}{50 \times 10^{-6}} - 40 - 20 + 30 = 0$$

$q = +1.5 \text{ mC}$  and the left plate is positive

- a. 1.5 mC, left plate is positive
- b. 1.5 mC, right plate is positive
- c. 0.50 mC, left plate is positive
- d. 0.50 mC, right plate is positive



10. Consider the circuit shown in the figure. What power is dissipated by the entire circuit?

$$R_1 = 3 + 4 + 3 = 10 \Omega$$

$$R_2 = \frac{10 \times 10}{10 + 10} = 5 \Omega, R_3 = 5 + 2 + 3 = 10 \Omega$$

$$R_4 = 5 \Omega, R_{tot} = 5 + 5 + 5 = 15 \Omega$$

$$W = \frac{28^2}{15} = 52.3 \text{ W}$$

- a. 14 W
- b. 28 W
- c. 52 W
- d. 112 W

