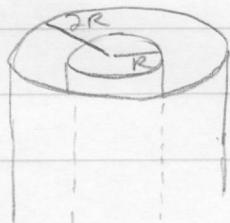


Physics 2b HW 8 Solutions Ch. 32 #7 p.1

two long solenoids of length l , radii $2R, R$, n turns/length w/ coincident axes, what is the mutual inductance?

$$M = \frac{\Phi_2}{I_1}$$



number of turns

$$\Phi_{2R} = \underbrace{n l B_R T R^2}_{\text{flux through one turn}}, \text{ flux through } 2R \text{ (note } B_R = 0 \text{ for } r > R)$$

$$B_R = \mu_0 n I_R \Rightarrow I_R = \frac{B_R}{\mu_0 n}, \text{ current in } R \text{ solenoid}$$

$$M = \frac{\Phi_{2R}}{I_R} = \frac{n l B_R T R^2}{B_R / \mu_0 n} = \boxed{\mu_0 n^2 l T R^2}$$

You should convince yourself that M is the same no matter which solenoid you call ① or ②.


$$\Phi_R = n l B_{2R} T R^2$$

$$B_{2R} = \mu_0 n I_{2R} \Rightarrow I_{2R} = \frac{B_{2R}}{\mu_0 n}$$

$$M = \frac{n l B_{2R} T R^2}{B_{2R} / \mu_0 n} = \boxed{\mu_0 n^2 l T R^2}$$

This should always be true.

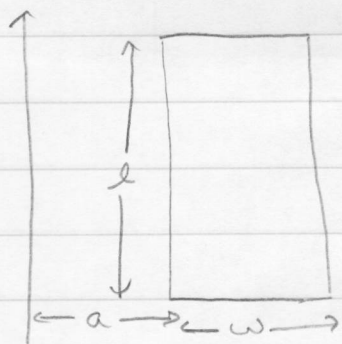Physics 2b HW 8 Solutions Ch. 32 # 9 p. 1



$$M = \frac{\phi_2}{I_1}$$

$$\phi_2 = \int B dA = \frac{\mu_0 I_1 l}{2\pi} \ln\left(\frac{a+w}{a}\right)$$

(check the last HW)

$$M = \frac{\mu_0 l \ln\left(\frac{a+w}{a}\right)}{2\pi}$$

#11

Solenoid, $l = 0.5\text{m}$, $R = 0.02\text{m}$, $n = 1000/0.5\text{m}$

What is the self inductance?

$$L = \frac{\phi}{I} = \frac{(n \cdot l)(\mu_0 n I)(\pi R^2)}{I} = \mu_0 n^2 l \pi R^2 = \boxed{3.16 \times 10^{-3} \text{H}}$$

\uparrow # turns \uparrow B \uparrow A

#22 Coaxial cable, inner radius a , outer radius b


What is the inductance per unit length? 2

$$\frac{L}{l} = \frac{\phi}{lI}$$

$$\phi = \int B dA = \int_{R=a}^{R=b} \frac{\mu_0 I}{2\pi R} l dR = \frac{\mu_0 I l}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$\frac{L}{l} = \frac{\mu_0}{2\pi} \ln\left(\frac{b}{a}\right)$$

Physics 2b HW8 Solutions Ch 32 # 33 p.1

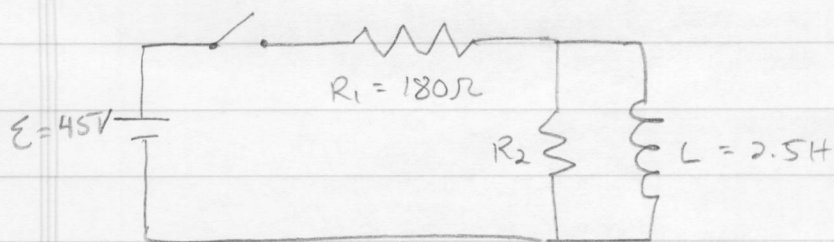

What is R_2 if $\mathcal{E}_{L, \max} = 100V$?

R_2 and L are in parallel \Rightarrow the voltage drop across them is the same. After the switch has been closed for a long time, the L acts as a wire and no voltage drops across R_2 (or L). The current is given by $I = \frac{\mathcal{E}}{R_1}$. When the switch is opened, the circuit

is effectively reduced to L and R_2 in series. The current cannot change instantaneously so all of I flows through $R_2 \Rightarrow$ the voltage drop is

$$IR_2 = \frac{\mathcal{E} R_2}{R_1} = \mathcal{E}_{L, \max} \Rightarrow R_2 = \frac{R_1 \mathcal{E}_{L, \max}}{\mathcal{E}} = \boxed{400\Omega}$$

#36 $\mathcal{E}_0 = 12V$, $R_1 = 4.0\Omega$, $R_2 = 8\Omega$, $R_3 = 2\Omega$, $L = 2.0H$

What is I_2 (a) when the switch is closed? (b) much later?

(c) when the switch is opened again?

The thing to keep in mind here is that I_3 cannot change instantaneously.

(a) $I_1 = I_2 = \mathcal{E}_0 / (R_1 + R_2) = 12V / (12\Omega) = \boxed{1A}$

(b) "a long time after" $\Rightarrow L$ is a wire

$$R_{\text{eff}} = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3}\right)^{-1} = 5.6\Omega$$

$$I_{\text{tot}} = \mathcal{E}_0 / R_{\text{eff}} = 12V / 5.6\Omega = 2.14A$$

$$I_2 R_2 = I_3 R_3 = (I_{\text{tot}} - I_2) R_3 \approx I_{\text{tot}} R_3 - I_2 R_3$$

$$\Rightarrow I_2 = \frac{I_{\text{tot}} R_3}{(R_2 + R_3)} = \boxed{1.6A}$$

(c) $I_2 = I_3 = I_{\text{tot}} - I_2 = \boxed{0.4A}$

Physics 2b HW8 Solutions Ch. 32 # 40 p. 1

$$L = 220 \times 10^{-3} \text{ H}, I = 350 \times 10^{-3} \text{ A}$$

How much energy must be supplied to raise I to 800 mA?

$$U = \frac{1}{2} LI^2 \Rightarrow \Delta U = \frac{1}{2} L (\Delta I)^2 = \frac{1}{2} (220 \times 10^{-3} \text{ H}) (800 \text{ mA} - 350 \text{ mA})^2 \\ = \boxed{2.23 \times 10^{-2} \text{ J}}$$

46

$$U = \frac{1}{2} LI^2 = \frac{1}{2} \mu_0 n^2 A l I^2 = \frac{1}{2} \mu_0 \left(\frac{N}{l}\right)^2 \pi \left(\frac{d}{2}\right)^2 l I^2$$

$$= \frac{1}{2} \mu_0 \left(\frac{500}{.23 \text{ m}}\right)^2 \pi \left(\frac{.015 \text{ m}}{2}\right)^2 .23 \text{ m} (65 \times 10^3 \text{ A})^2$$

$$= \boxed{7.85 \times 10^{-6} \text{ J}}$$

55


A toroidal coil, inner radius R , square $l \times l$ cross-section

N turns of wire, current I . What is the magnetic energy?


$$U = \int u_B dV = \int \frac{B^2}{2\mu_0} dV = \frac{1}{2\mu_0} \int_{r=R}^{r=R+l} \left(\frac{\mu_0 N I}{2\pi r}\right)^2 \cdot 2\pi r l dr \quad \leftarrow \text{Eq 30-12}$$
$$= \frac{\mu_0^2 N^2 I^2 l}{2\mu_0 2\pi} \int_{r=R}^{r=R+l} \frac{1}{r} dr$$

$$= \boxed{\frac{\mu_0 N^2 I^2 l}{4\pi} \ln\left(\frac{R+l}{R}\right)}$$

Physics 2b HW8 Solutions Ch. 32 #66 p.1


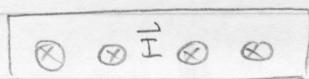


$\vec{B} = ?$

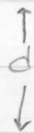

$$B = \frac{\mu_0 J_s}{2} + \frac{\mu_0 J_s}{2} = \mu_0 J_s = \frac{\mu_0 I}{w}$$

(Note that they add by right hand rule)

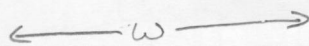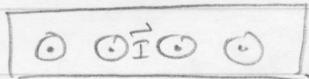

$$\frac{U}{l} = \frac{u_B V}{l} = \frac{B^2}{2\mu_0} dw = \left(\frac{\mu_0 I}{w} \right)^2 \frac{dw}{2\mu_0}$$

$$= \frac{1}{2} \mu_0 I^2 \frac{dw}{w}$$

$$U = \frac{1}{2} L I^2 = \frac{1}{2} \left(\mu_0 \frac{dl}{w} \right) I^2 \Rightarrow \frac{L}{l} = \boxed{\frac{\mu_0 d}{w}}$$

Physics 2b HW 8 Solutions Ch. 33 # 7 p.1


$$V = V_p \sin \omega t$$

$$V_{rms}^2 \equiv \frac{1}{\tau} \int_{t=0}^{t=\tau} v^2 dt = \frac{1}{\tau} \int_0^{\tau} V_p^2 \sin^2(\omega t) dt$$

$$= \frac{V_p^2}{\tau} \left(\frac{t}{2} - \frac{\sin(2\omega t)}{4\omega} \right) \quad \omega\tau = 2\pi$$

$$= \frac{V_p^2}{2} \Rightarrow \boxed{V_{rms} = \frac{V_p}{\sqrt{2}}}$$

#9

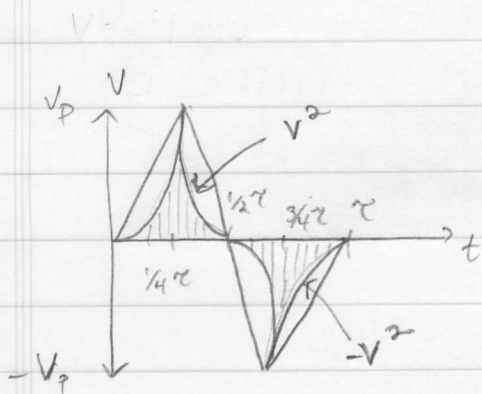

$$\int_0^{\tau} v^2 dt = 4 \int_0^{\tau/4} v^2 dt = 4 \int_0^{\tau/4} \left(\frac{4V_p}{\tau} t \right)^2 dt$$

$$= 4 \left(\frac{4V_p}{\tau} \right)^2 \frac{1}{3} \left(\frac{\tau}{4} \right)^3$$

$$= \frac{1}{3} V_p^2 \tau$$

$$V_{rms}^2 = \frac{1}{3} V_p^2 \Rightarrow \boxed{V_{rms} = \frac{V_p}{\sqrt{3}}}$$

$$\#11 \quad I_1 \sin(\omega t) + I_2 \cos(\omega t) = I_p \sin(\omega t + \phi)$$

must be true at all times \Rightarrow consider $t=0$ and $t=\pi/2$

$$\omega t=0 \Rightarrow I_2 = I_p \sin(\phi)$$

$$\omega t=\pi/2 \Rightarrow I_1 = I_p \sin(\pi/2 + \phi) = I_p \cos(\phi)$$

$$\sin^2 \phi + \cos^2 \phi = \left(\frac{I_2}{I_p} \right)^2 + \left(\frac{I_1}{I_p} \right)^2 = 1 \Rightarrow \boxed{I_p = \sqrt{I_1^2 + I_2^2}}$$

$$\frac{\sin \phi}{\cos \phi} = \tan \phi = \frac{(I_2/I_p)}{(I_1/I_p)} = \frac{I_2}{I_1} \Rightarrow \boxed{\phi = \tan^{-1}(I_2/I_1)}$$

Physics 2b HW 8 Solutions | Ch. 33 #17 p.1

$$I_p = V_p \omega C = \frac{V_p}{R} \Rightarrow C = \frac{1}{R\omega} = \boxed{1.47 \times 10^{-6} \text{ F}}$$

#20

$$X_C = 1 \times 10^3 \Omega, \quad C = 2 \times 10^{-6} \text{ F}$$

$$X_C = \frac{1}{\omega C} \Rightarrow \omega = \frac{1}{X_C C} = 500 \text{ rad/s} = \boxed{79.6 \text{ Hz}}$$

$$X_L = \omega L \Rightarrow L = \frac{X_L}{\omega} = \frac{1 \times 10^3 \Omega}{500 \text{ rad/s}} = \boxed{2 \text{ H}}$$

$$\frac{X_C}{X_L} \approx \frac{1}{\omega^2} \Rightarrow \boxed{X_L' = 4 X_C'}$$

#24

$$\omega = 2\pi \times 10 \times 10^3 \text{ Hz}$$

$$X_L = 10 X_C$$

$$\omega L = \frac{10}{\omega C} \Rightarrow CL = \frac{10}{\omega^2}$$

$$X_L' = X_C'$$

$$\omega' L = \frac{1}{\omega' C} \Rightarrow \omega' = \sqrt{\frac{1}{CL}} = \frac{\omega}{\sqrt{10}} \Rightarrow f' = \frac{\omega}{2\pi\sqrt{10}} = \boxed{3.16 \times 10^3 \text{ Hz}}$$

#37

Eqs in section 33-3 (note $\frac{\omega\tau}{8} = 45^\circ$)

$$(a) q(t) = q_{sp} \cos(\omega t) \Rightarrow q(\tau/8) = q_{sp} \cos(\omega \tau/8)$$

$$q/q_{sp} = \boxed{1/\sqrt{2}}$$

$$(b) U_E/U_{E,p} = \cos^2(\omega \tau/8) = \boxed{1/2}$$

$$(c) I/I_p = -\sin(\omega \tau/8) = \boxed{-1/\sqrt{2}}$$

$$(d) U_B/U_{B,p} = \sin^2(\omega \tau/8) = \boxed{1/2}$$