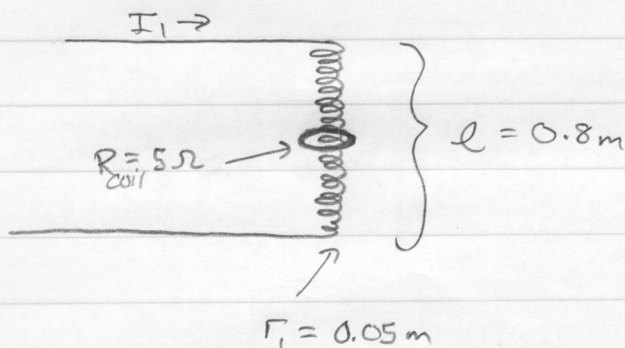


Physics 2b Quiz 8 Solutions #1

$L = 18 \text{ mH}$ ,  $l = 0.8 \text{ m}$ ,  $r_1 = 0.05 \text{ m}$

$R_{\text{coil}} = 5 \Omega$ ,  $M = 60 \mu\text{H}$ ,  $I_1 = 300 \text{ mA}$ ,  $\frac{dI_1}{dt} = -2.5 \text{ A/s}$



What is  $I_{\text{coil}}$  when  $dI_1/dt = -2.5 \text{ A/s}$ ?


$$\mathcal{E}_{\text{coil}} = -M \frac{dI_1}{dt} = -60 \mu\text{H} (-2.5 \text{ A/s}) = 1.5 \times 10^{-4} \text{ V}$$

$$\text{Ohm's law} \Rightarrow I = \frac{\mathcal{E}_{\text{coil}}}{R_{\text{coil}}} = \frac{1.5 \times 10^{-4} \text{ V}}{5 \Omega} = \boxed{30 \mu\text{A}}$$
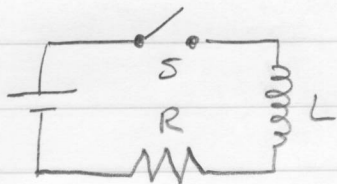
#2

$\mathcal{E} = 60 \text{ V}$ ,  $L = 30 \text{ H}$ ,  $R = 12 \Omega$


What is  $I$  when  $t = 3.5 \text{ s}$ ? ( $t$  measured after switch closes)



$$\begin{aligned} I(t) &= I_0 (1 - e^{-R/L t}) \\ &= \frac{\mathcal{E}_0}{R} (1 - e^{-R/L t}) \\ &= \frac{60 \text{ V}}{12 \Omega} (1 - e^{-\frac{12 \Omega}{30 \text{ H}} (3.5 \text{ s})}) \\ &= 3.76 \text{ A} \Rightarrow \boxed{3.8 \text{ A}} \end{aligned}$$
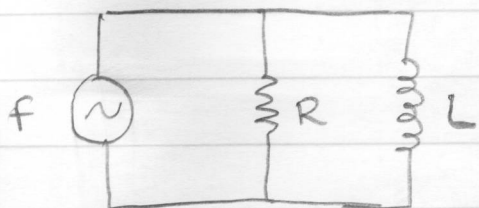
### Physics 2b Quiz 8 Solutions # 3

$$R = 300 \Omega, L = 250 \text{ mH}, f = 100 \text{ Hz}, I_{\text{rms},L} = 0.5 \text{ A}$$



What is  $I_{\text{rms},R}$ ?

Because we have an AC source, we can assume a voltage of the form  $V(t) = V_p \sin(\omega t)$  where  $\omega = 2\pi f$ . Notice that  $R$  and  $L$  are in parallel with the AC source, so the voltage across both  $R$  and  $L$  is equal to the source voltage at all times. Since we are looking for a time averaged quantity,  $I_{\text{rms},R}$ , we can treat  $L$  as a resistor with resistance  $X_L = \omega L$  in this simple case.

$$\begin{aligned} \text{Ohm's law} \Rightarrow V_{\text{rms},L} &= I_{\text{rms},L} X_L \\ &= (0.5 \text{ A})(2\pi(100 \text{ Hz}))(250 \text{ mH}) \\ &= 78.54 \text{ V} \end{aligned}$$


$$\text{From above, } V_{\text{rms},L} = V_{\text{rms},R}$$

$$\text{Ohm's law} \Rightarrow I_{\text{rms},R} = \frac{V_{\text{rms},R}}{R} = \frac{78.54 \text{ V}}{300 \Omega} = \boxed{0.26 \text{ A}}$$

## Physics 2b Quiz 8 Solutions #4

$$F = 60 \text{ Hz}, V_p = 120 \text{ V}, X_C = 900 \Omega, X_L = 300 \Omega$$

$$R = 400 \Omega$$

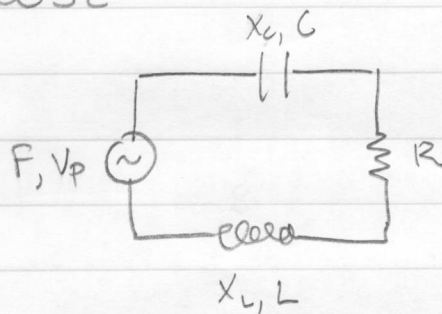

What is  $L$ ?

$$X_L = \omega L \Rightarrow L = \frac{X_L}{\omega} = \frac{X_L}{2\pi F} = \frac{300 \Omega}{2\pi (60 \text{ Hz})} = .796 \text{ H}$$

$$\Rightarrow \boxed{800 \text{ mH}}$$

## #5

This is an extension of the analogy presented in class and detailed in Table 33-3.

The key to this question is to realize that

$q$  and  $x$  are analogous, therefore  $\dot{q} = I$  and  $\dot{x} = v$  are also analogous. Kinetic energy is  $\frac{1}{2}mv^2$

so you should look for an energy with  $I^2$ ,

which is  $U = \frac{1}{2}LI^2$ , the magnetic energy stored in the inductor.