

PHYSICS 4C: QUIZ 3 SOLUTIONS

PROBLEM 1

In equilibrium, the two spheres are at the same potential

$$(1) \quad V = \frac{kQ_1}{R_1} = \frac{kQ_2}{R_2},$$

The total charge on the surfaces of the two spheres is Q , so:

$$(2) \quad Q_2 = Q - Q_1.$$

Plugging this into equation (1) and rearranging,

$$(3) \quad Q_1 = \frac{QR_1}{R_1 + R_2}.$$

PROBLEM 2

No work done means the potential at points A and B is the same. The potentials are

$$(4) \quad V_A = k \left(\frac{30\mu\text{C}}{30\text{cm}} - \frac{10\mu\text{C}}{20\text{cm}} \right) = 0.5k \frac{\mu\text{C}}{\text{cm}}$$

$$(5) \quad V_B = k \left(\frac{30\mu\text{C}}{L \text{ cm}} - \frac{10\mu\text{C}}{(L + 50)\text{cm}} \right)$$

Setting them equal to each other and canceling k and units,

$$(6) \quad \frac{30}{L} - \frac{10}{L + 50} = 0.5$$

$$(7) \quad L^2 + 10L - 3000 = 0$$

$$(8) \quad L = -5 \pm 55$$

The negative sign gives a solution to the right of q_2 , so we choose the positive, $L = 50\text{cm}$.

PROBLEM 3

The equivalent capacitance of C_2 and C_3 (series) is

$$(9) \quad C_a = \left(\frac{1}{2C} + \frac{1}{C} \right)^{-1} = \frac{2C}{3}.$$

The equivalent capacitance of C_a and C_4 (parallel) is

$$(10) \quad C_b = \frac{2C}{3} + 2C = \frac{8C}{3}.$$

The equivalent capacitance of the circuit is the equivalent capacitance of C_b and C_1 (series),

$$(11) \quad C_{circuit} = \left(\frac{3}{8C} + \frac{1}{C} \right)^{-1} = \frac{8C}{11}.$$

For the second part, we can write down the following equations for voltages, using the same equivalent capacitors as before:

$$(12) \quad V_1 + V_b = V, \text{ and}$$

$$Q_1 = Q_b$$

$$C_1 V_1 = C_b V_b$$

$$(13) \quad C V_1 = \frac{8C V_b}{3}.$$

Eliminating V_1 between equations (12) and (13) and solving for V_b ,

$$(14) \quad V_b = \frac{3V}{11}.$$

Next, we find V_2 from V_b :

$$(15) \quad V_2 + V_3 = V_b = \frac{3V}{11}$$

$$Q_2 = Q_3$$

$$C_2 V_2 = C_3 V_3$$

$$(16) \quad 2C V_2 = C V_3.$$

Eliminating V_3 between equations (15) and (16) and solving for V_2 ,

$$(17) \quad V_2 = \frac{V_b}{3} = \frac{V}{11}$$

$$(18) \quad Q_2 = C_2 V_2 = \frac{2CV}{11}.$$

PROBLEM 4

The two halves of the capacitor act as two capacitors in parallel, each of area $A/2$. Their capacitances add:

$$(19) \quad C = C_1 + C_2 = (K_1 + K_2) \frac{\epsilon_0 A}{2d}.$$