

## PHYSICS 4C: QUIZ 5 SOLUTIONS

### PROBLEM 1

The total voltage drop for any loop is 0, so

$$(1) \quad V = \frac{Q}{C} + V_R$$

for either capacitor and either resistor. Specifically, the voltage drop over  $R_1$  at the instant when  $Q_1 = 7\mu\text{C}$  is

$$(2) \quad V_{R_1} = V - \frac{Q_1}{C_1} = 12\text{V} - \frac{7\mu\text{C}}{1.8\mu\text{F}} = 8.11\text{V}$$

and the current through it is

$$(3) \quad I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{8.11\text{V}}{1.8\text{k}\Omega} = 4.5\text{mA}$$

**Alternative solution.** The equivalent resistance is  $R_{eq} = 1.35\text{k}\Omega$  (in parallel, inverses of resistances add). The equivalent capacitance is  $C_{eq} = 7.2\mu\text{F}$  (in parallel, capacitances add). The voltage drop over the two capacitors is the same,

$$(4) \quad V_C = \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{Q_{eq}}{C_{eq}},$$

so we can solve for the charge on the equivalent capacitor:

$$(5) \quad Q_{eq} = \frac{Q_1 C_{eq}}{C_1} = 28\mu\text{C}$$

Now we use the formula for charging the equivalent capacitor

$$(6) \quad Q_{eq} = C_{eq}V \left(1 - e^{-t/R_{eq}C_{eq}}\right),$$

from which we can solve for time:

$$(7) \quad t = -R_{eq}C_{eq} \ln \left(1 - \frac{Q_{eq}V}{C_{eq}}\right) = 0.0038\text{s}.$$

Dividing both sides of equation (6) by  $C_{eq}$ , we can solve for the voltage drop across the capacitors:

$$(8) \quad V_C = V \left(1 - e^{-t/R_{eq}C_{eq}}\right),$$

from which we find the voltage drop across the resistors

$$(9) \quad V_R = V - V_C = V e^{-t/R_{eq}C_{eq}} = 8.11\text{V}$$

and current through the first resistor

$$(10) \quad I_{R_1} = \frac{V_R}{R_1} = \frac{8.11\text{V}}{1.8\text{k}\Omega} = 4.5\text{mA}$$

#### PROBLEM 2

Adding resistors in series for each branch and replacing them by equivalent resistances, we get  $I_1$  flowing through  $R_1 = 19\Omega$ ,  $I_2$  flowing through  $R_2 = 12\Omega$ , and  $I_3$  flowing through  $R_3 = 35\Omega$ . The current going into and out of a node is the same:

$$(11) \quad I_1 = I_2 + I_3$$

The voltage drop is 0 over any closed loop, so for the top loop,

$$(12) \quad 6\text{V} - (19\Omega)I_1 + 12\text{V} - (12\Omega)I_2 = 0$$

and for the outer loop,

$$(13) \quad 6\text{V} - (19\Omega)I_1 + 12\text{V} - (35\Omega)I_3 = 0$$

Solving these three equations for the three unknowns, we get

$$(14) \quad I_1 = 0.64\text{A}, I_2 = 0.48\text{A}, I_3 = 0.16\text{A}$$

#### PROBLEM 3

$$(15) \quad F = ma = \frac{mv^2}{R} = 3.1 \times 10^{-4}\text{N}$$

$$(16) \quad B = \frac{F}{qv} = 0.023\text{T}$$

$$(17) \quad f = \frac{1}{T} = \frac{v}{2\pi R} = 3 \times 10^3\text{Hz}$$

#### PROBLEM 4

$$(18) \quad F = I\vec{l} \times \vec{B}$$

When the wire is along  $x$ -axis,

$$(19) \quad F_1 = Il\hat{i} \times \vec{B} = 5 \left( B_y\hat{k} - B_z\hat{j} \right) = -2.5\hat{j}$$

When the wire is along  $y$ -axis,

$$(20) \quad F_2 = Il\hat{j} \times \vec{B} = 5 \left( B_z\hat{i} - B_x\hat{k} \right) = 2.5\hat{i} - 5\hat{k}$$

Setting vector components in the same direction equal to each other,

$$(21) \quad B_x = 1\text{T}, B_y = 0, B_z = 0.5\text{T}$$