

PHYSICS 110A : CLASSICAL MECHANICS
MIDTERM EXAM #1

[1] A particle of mass m moves in the one-dimensional potential

$$U(x) = \frac{U_0}{a^4} (x^2 - a^2)^2 . \quad (1)$$

(a) Sketch $U(x)$. Identify the location(s) of any local minima and/or maxima, and be sure that your sketch shows the proper behavior as $x \rightarrow \pm\infty$.

[15 points]

(b) Sketch a representative set of phase curves. Be sure to sketch any separatrices which exist, and identify their energies. Also sketch all the phase curves for motions with total energy $E = \frac{1}{2}U_0$. Do the same for $E = 2U_0$.

[15 points]

(c) The phase space dynamics are written as $\dot{\varphi} = \mathbf{V}(\varphi)$, where $\varphi = \begin{pmatrix} x \\ \dot{x} \end{pmatrix}$. Find the upper and lower components of the vector field \mathbf{V} .

[10 points]

(d) Derive an expression for the period T of the motion when the system exhibits small oscillations about a potential minimum.

[10 points]

[2] An R - L - C circuit is shown in fig. 1. The resistive element is a light bulb. The inductance is $L = 400 \mu\text{H}$; the capacitance is $C = 1 \mu\text{F}$; the resistance is $R = 32 \Omega$. The voltage $V(t)$ oscillates sinusoidally, with $V(t) = V_0 \cos(\omega t)$, where $V_0 = 4 \text{ V}$. In this problem, you may neglect all transients; we are interested in the late time, steady state operation of this circuit. Recall the relevant MKS units:

$$1 \Omega = 1 \text{ V} \cdot \text{s} / \text{C} \quad , \quad 1 \text{ F} = 1 \text{ C} / \text{V} \quad , \quad 1 \text{ H} = 1 \text{ V} \cdot \text{s}^2 / \text{C} .$$

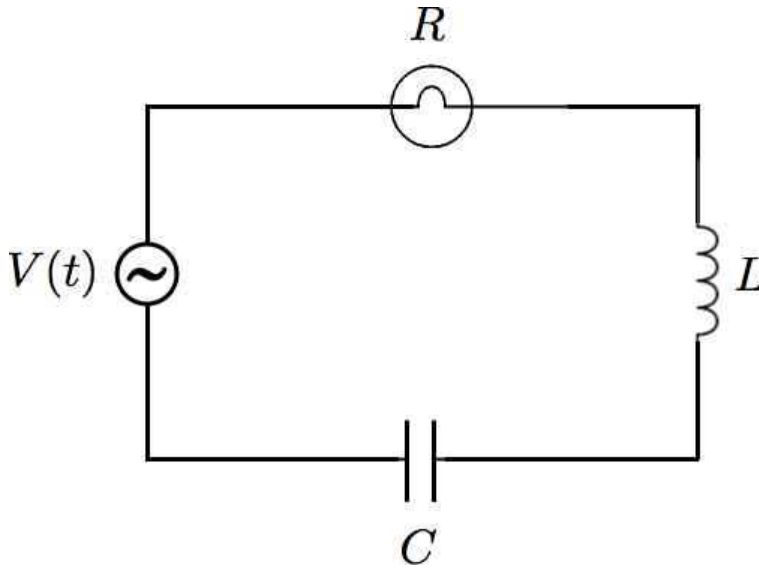


Figure 1: An R - L - C circuit in which the resistive element is a light bulb.

(a) Is this circuit underdamped or overdamped?

[10 points]

(b) Suppose the bulb will only emit light when the average power dissipated by the bulb is greater than a threshold $P_{\text{th}} = \frac{2}{9} \text{ W}$. For fixed $V_0 = 4 \text{ V}$, find the frequency range for ω over which the bulb emits light. Recall that the instantaneous power dissipated by a resistor is $P_R(t) = I^2(t)R$. (Average this over a cycle to get the average power dissipated.)

[20 points]

(c) Compare the expressions for the instantaneous power dissipated by the voltage source, $P_V(t)$, and the power dissipated by the resistor $P_R(t) = I^2(t)R$. If $P_V(t) \neq P_R(t)$, where does the extra power go or come from? What can you say about the averages of P_V and $P_R(t)$ over a cycle? Explain your answer.

[20 points]