

PHYSICS 110A : CLASSICAL MECHANICS
MIDTERM EXAM #1

[1] A particle of mass m moves in the one-dimensional potential

$$U(x) = k(x^2 - a^2)e^{-x/a} . \quad (1)$$

- (a) What are the dimensions of the constants k and a ?
- (b) Sketch $U(x)$. Identify the location(s) of any local minima and/or maxima, and be sure that your sketch shows the proper behavior as $x \rightarrow \pm\infty$.
- (c) Sketch a representative set of phase curves. Identify any and all fixed points, find their energies, and assess their stability. Find the energy of every separatrix.
- (d) Find the frequency of small oscillations about the minimum of $U(x)$.

[2] Consider the electrical circuit depicted below. The inductance is $L = 1$ mH and the capacitances are $C_1 = 100 \mu\text{F}$ and $C_2 = 150 \mu\text{F}$. The system is forced by a time-dependent voltage source $V(t) = V_0 \cos(\Omega t)$, where $V_0 = 8$ mV and $\Omega = 10^3 \text{ s}^{-1}$. The charge Q_1 on the upper plate of capacitor C_1 is found to lead the voltage source $V(t)$ (*i.e.* the difference in potential between the upper and lower termini of the source in the figure) by a phase angle $\delta = \frac{\pi}{4}$. Recall the relevant MKS units: $1 \Omega = 1 \text{ V} \cdot \text{s} / \text{C}$, $1 \text{ F} = 1 \text{ C} / \text{V}$, and $1 \text{ H} = 1 \text{ V} \cdot \text{s}^2 / \text{C}$.

- (a) The voltage drops across the two capacitors are the same. Use this fact to express Q_1 in terms of the total charge $Q = Q_1 + Q_2$. Do the same for Q_2 .
- (b) Write down the equation of motion for $Q(t)$.
- (c) What is the value of the resistance R ?
- (d) Find the current $I(t)$ flowing through the resistor. Your expression should involve no unknown quantities other than the time variable t .

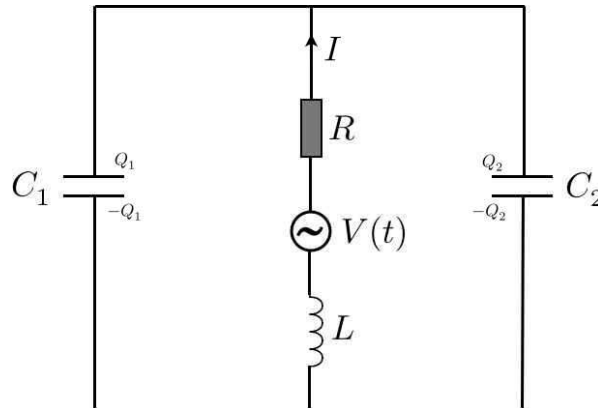


Figure 1: The circuit for problem 2.