
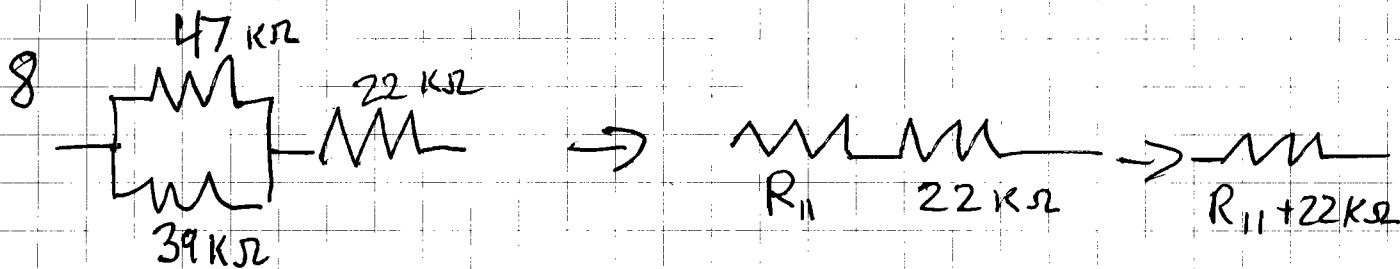


28 4

$$E = 9V \Rightarrow V = 9V$$

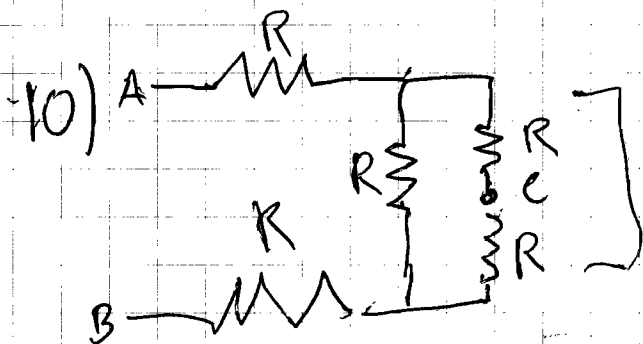


$$\frac{1}{R_{11}} = \frac{1}{47} + \frac{1}{39} \quad R = \frac{1}{\frac{1}{47} + \frac{1}{39}} + 22$$




$$2R \quad \frac{1}{\frac{1}{2R} + \frac{1}{R}} = \frac{2}{3}R$$

a)  $R_{eff} = \frac{8}{3}R \quad A \rightarrow B$

b)  $I = \frac{V}{R_{eff}}$

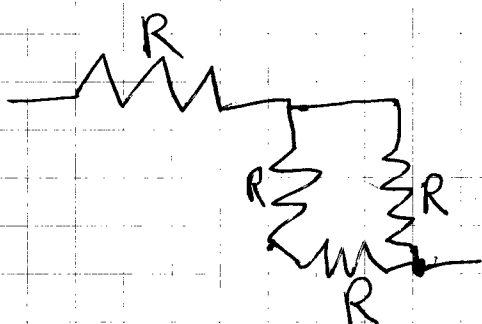


$$R + \frac{2}{3}R = \frac{5}{3}R$$

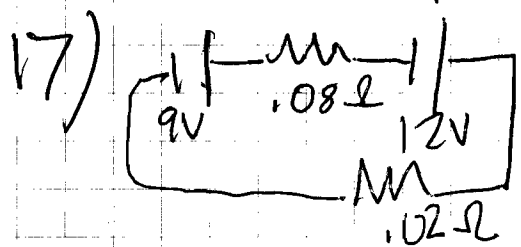

$$V = 21V \quad R = .1\Omega$$

$$I = \frac{V}{R} = 210 \text{ amps}$$

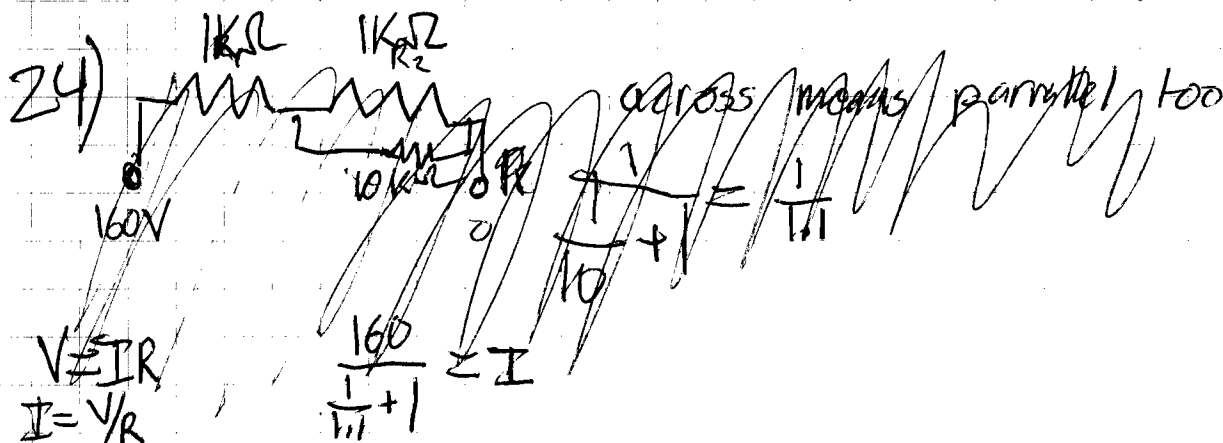


$$V = IR$$

$$I = \frac{V}{R}$$


24)

across means parallel too

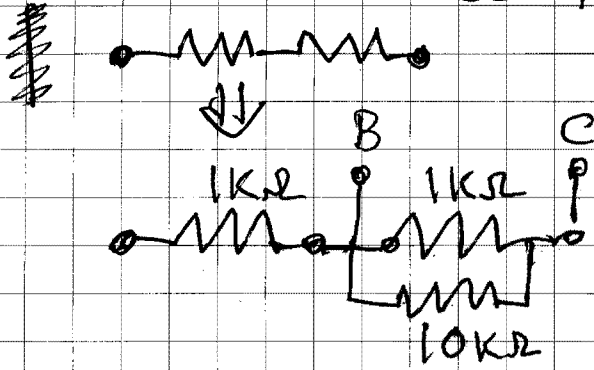

$$V = IR_{\text{eff}} \quad R_{\text{eff}} = 1 + \frac{1}{\frac{1}{10} + 1} \text{ k}\Omega = 1.9 \text{ k}\Omega$$
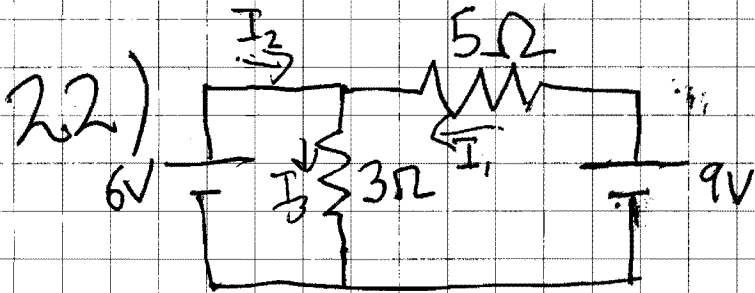
$$V_{BC} = IR_{BC} = I \cdot 91 = \frac{V \cdot 91}{1.91}$$



$$I_3 = I_1 + I_2$$

$$6 - (I_1 + I_2)3 = 0$$

$$9 - 5I_1 - 3(I_1 + I_2) = 0$$

$$3 - 5I_1 = 0 \quad I_1 = \frac{3}{5} \text{ V}$$


$$6 - \frac{9}{5} - 3I_2 = 0$$




$$21 - 5I_2 = 0 \quad I_2 = \frac{7}{5} \text{ V} \quad I_3 = 2 \text{ amps}$$

$$7 - 5I_2 = 0$$

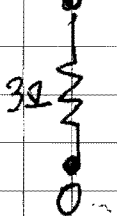6V (from the battery) which is what you would get by noting



$$\Rightarrow I = 2 \text{ amps}$$

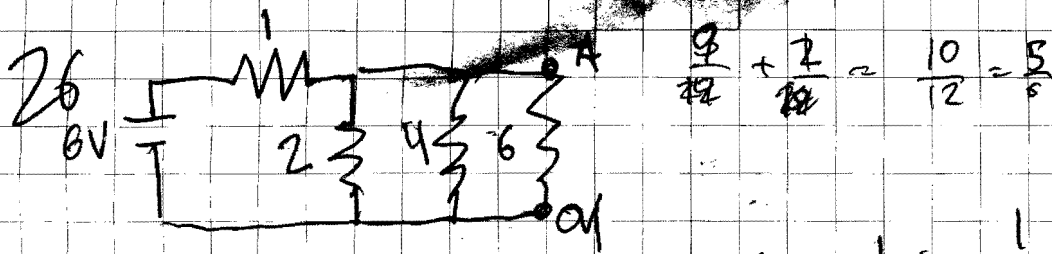


$$\frac{9}{12} + \frac{2}{12} = \frac{10}{12} = \frac{5}{6}$$

$$R_{\text{eff}} = 1 + \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{6}} = 1 + \frac{1}{\frac{5}{6}} = 1 + \frac{6}{5} = \frac{11}{5}$$

$$V = IR \Rightarrow I = \frac{6}{\frac{11}{5}} = \frac{30}{11} \text{ amps}$$

$$V_A = 6 - \frac{30}{11} \text{ amp} \cdot 1 \Omega = \frac{36}{11} \text{ V}$$
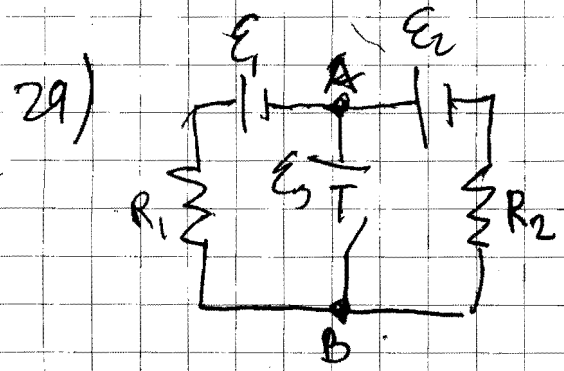
$$I = \frac{36}{11} \text{ V} / 6 \Omega = \frac{6}{11} \text{ amps}$$





to make the circuits the same the voltage drop across the  $E_3$  battery (A  $\rightarrow$  B) must be  $E_3$  with the switch open

let B be at 0V 
$$I = \frac{E_1 + E_2}{R_1 + R_2}$$

$$E_1 - R_1 \left( \frac{E_1 + E_2}{R_1 + R_2} \right) = E_3$$

Voltage change from A  $\rightarrow$  B

3)

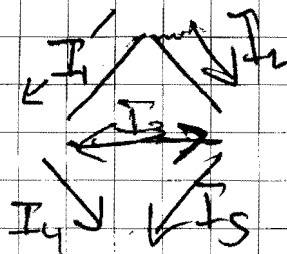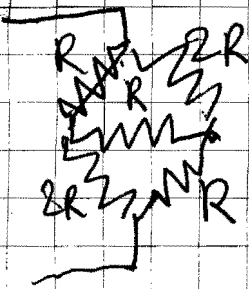

based on symmetry  
 $I_1 = I_5$   $I_2 = I_4$

long way

$$\underline{I_4 + I_3 = I}$$

$$I_1 = I_3 + I_2$$

$$V - I_1 R - I_2 (2R) = 0$$

$$I_1 R + I_3 R - I_2 (2R) = 0$$

$$\begin{pmatrix} -1 & 1 & 1 \\ -R & -2R & 0 \\ R & R & -2R \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ V \\ 0 \end{pmatrix} \Rightarrow \begin{pmatrix} -1 & 1 & 1 \\ -1 & -2 & 0 \\ 1 & 1 & -2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ V/R \\ 0 \end{pmatrix}$$

inverting this gives


$$I_1 = \frac{+3V}{5R} \quad I_2 = \frac{V}{5R} \quad I_3 = \frac{2V}{5R} \quad \text{so } I = I_1 + I_2$$

$$= \frac{V}{R} \Rightarrow R_{\text{eff}} = R$$

short way: there are 3 paths with total resistance  $3R$

$$\frac{1}{3R} + \frac{1}{2R} + \frac{1}{3R} = \frac{1}{R_{\text{eff}}} = \frac{1}{R} \Rightarrow R_{\text{eff}} = R$$

(this method has limited use)

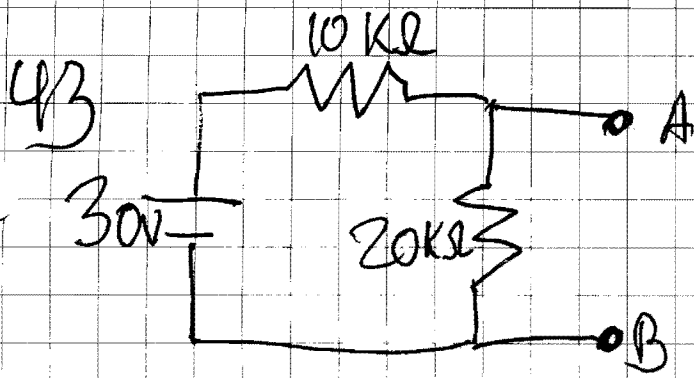


$$I = 1 \text{ mA}$$

a)  $20 \text{ V}$

b)  $0$  amps (Ammeters must be hooked up in series)

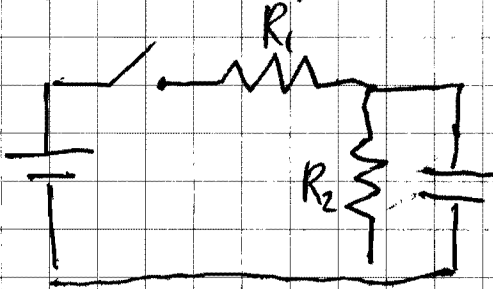55)  $\mathcal{E} = 100$   $R_1 = 4 \text{ k}\Omega$   $R_2 = 6 \text{ k}\Omega$



$$I_1 = 25 \text{ mA}$$

$$I_2 = 0$$

a) When the switch is closed all the current goes through the capacitor

since the voltage drop across the capacitor is  $Q/C$  and there is no charge yet

b) once the capacitor is fully charged no current can flow to it

$$I_1 = I_2 = 10 \text{ mA} \quad (\text{note } V_C = 60 \text{ V})$$

c) once the switch opens  $R_1$  is out of the circuit and the capacitor

$$V_C = 60 \text{ V} \quad R = 6 \text{ k}\Omega \Rightarrow I = 10 \text{ mA}$$

d) along time later  $V_C = 0 \Rightarrow Q = 0$  so  $I = 0$