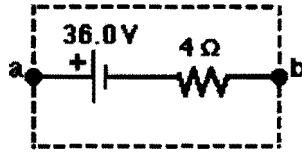


Name_Professor S.K. Sinha_____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.


Figure 26.1



The emf and the internal resistance of a battery are as shown.


1) In Figure 26.1, when the terminal voltage V_{ab} is equal to 31.6 V, the current through the battery, including direction, is closest to:

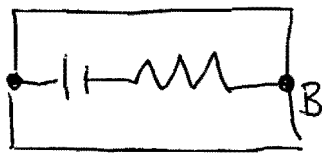- A) 1.2 A, from a to b
- B) 1.3 A, from b to a
- C) 1.1 A, from a to b
- D) 1.1 A, from b to a**
- E) 1.2 A, from b to a



assume current goes from B to A
 $-I \cdot 4\Omega + 36.0V = 31.6V$

Figure 27.1

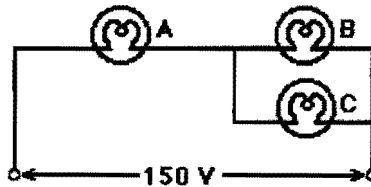

$I \cdot 4\Omega = 4.4V$
 $I = 1.1 \text{ amps}$
 since it is positive we chose direction correctly

Three light bulbs, A, B, and C, have electrical ratings as follows:

- Bulb A - 96 W, 2.0 A
- Bulb B - 200 V, 250 W
- Bulb C - 120 V, 0.5 A

The three bulbs are connected in a circuit, which is across a 150-V line, as shown. Assume the filament resistances of the light bulbs are constant and independent of operating conditions.

2) In Figure 27.1, the current through bulb B is closest to:

- A) 0.75 A**
- B) 1.25 A
- C) 1.00 A
- D) 1.10 A
- E) 0.85 A

light bulbs are basically just resistors, and we need to find what they are
 $P = I^2 R = \frac{V^2}{R}$

$V = IR$

$96 = 4 \cdot R_A$

$R_A = 24\Omega$

$250 = \frac{40000}{R_B}$

$R_B = 160\Omega$


$120 = .5 R_C$
 $I_A = I_{total} = \frac{150}{120}$

$R_C = 240\Omega$
 $V_p = 150 - I_{total} R_A = 120$



$R_{eff} = 24 + \frac{1}{\frac{1}{160} + \frac{1}{240}} = 120$

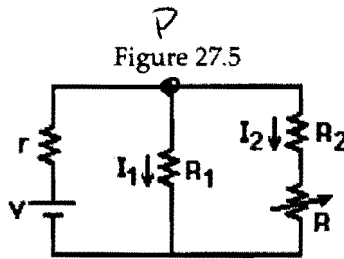$\Delta V_B = 120$
 $R_B = 160 \Rightarrow I = .75$



3) In Figure 27.5, the circuit R is a variable resistance. As R is decreased

- A) ~~I_1 decreases, I_2 decreases.~~
- B) I_1 decreases, I_2 increases.
- C) ~~I_1 increases, I_2 decreases.~~
- D) ~~I_1 remains unchanged, I_2 increases.~~
- E) ~~I_1 increases, I_2 increases.~~


as R decreases the resistance of the pieces in parallel decreases thus the total resistance decreases which increases the net current and thus by ohm's law the voltage at point P is decreased (greater $I =$ greater voltage drop across r)

V_p decreases so I_1 decreases

~~so what matters~~

~~is then does I_2 increase even though~~

Figure 27.10

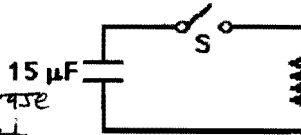

note that since I_1 is now lower than before but I_{tot} is higher and $I_1 + I_2 = I_{tot}$ I_2 must have increased

Initially, for the circuit shown, the switch S is open and the capacitor voltage is 80 V. The switch S is closed at time $t = 0$.

4) In Figure 27.10, the charge on the capacitor, when the current in the circuit is $33 \mu A$, in μC , is closest to:

- A) 1000
- B) 900
- C) 950
- D) 850
- E) 800

$$V(t) = V_0 e^{-t/RC} \Rightarrow \text{from } \cancel{R} \dot{Q}(t) + \frac{Q(t)}{C} = 0$$

$$\text{and } V(t) = \frac{Q(t)}{C} = R \dot{Q}(t)$$

$$I(t) = \frac{V(t)}{R}$$

$$33 \mu A = \frac{80}{2 \times 10^6} e^{-t/RC} \Rightarrow e^{-t/RC} = \frac{33 \times 10^{-6} \cdot 2 \times 10^6}{80}$$

$$Q(t) = Q_0 e^{-t/RC} = C V_0 e^{-t/RC}$$

$$Q(t) = \frac{15 \times 10^{-6} \cdot 80 \cdot 33 \cdot 2}{80} (\times 10^6) = 990 \mu C \text{ not } C$$